

Electronics Equations

For Resistors in series:

$$\mathbf{R_{total} = R_1 + R_2 + R_3 + ..}$$

For Resistors in parallel:

$$\frac{1}{\mathbf{R_{total}}} = \frac{1}{\mathbf{R_1}} + \frac{1}{\mathbf{R_2}} + \frac{1}{\mathbf{R_3}} + ..$$

Voltage and Current Relationships:

$$\mathbf{V = I \cdot R} \quad \mathbf{I = \frac{V}{R}} \quad \mathbf{R = \frac{V}{I}}$$

Capacitors in series:

$$\frac{1}{\mathbf{C_{total}}} = \frac{1}{\mathbf{C_1}} + \frac{1}{\mathbf{C_2}} + \frac{1}{\mathbf{C_3}} + ..$$

Capacitors in parallel:

$$\mathbf{C_{total} = C_1 + C_2 + C_3 + ...}$$

Impedance of an RC circuit:

$$\mathbf{Z = \frac{1}{2 \cdot \pi \cdot f \cdot R \cdot C}} \quad \mathbf{Z = \frac{1}{\omega \cdot R \cdot C}}$$

Charging an RC Circuit:

$$i(t) = \frac{V_{in}}{R} \cdot e^{-\left(\frac{t}{R \cdot C}\right)}$$

$$V_R(t) = V_{in} \cdot e^{-\left(\frac{t}{R \cdot C}\right)}$$

$$V_C(t) = V_{in} \cdot \left[1 - e^{-\left(\frac{t}{R \cdot C}\right)} \right]$$

Low Pass Filter:

$$A = \frac{1}{\sqrt{\omega^2 \cdot R^2 \cdot C^2 + 1}}$$

$$\phi = -\tan^{-1} \cdot \left(\frac{-1}{\omega \cdot R \cdot C} \right) - \frac{\pi}{2}$$

$$A = \frac{1}{\sqrt{(2 \cdot \pi \cdot f \cdot R \cdot C)^2 + 1}}$$

$$\phi = -\text{atan} \cdot \left(\frac{-1}{2 \cdot \pi \cdot f \cdot R \cdot C} \right) - \frac{\pi}{2}$$

High Pass Filter:

$$A = \frac{\omega \cdot R \cdot C}{\sqrt{\omega^2 \cdot R^2 \cdot C^2 + 1}}$$

$$\phi = \text{atan} \cdot \left(\frac{1}{\omega \cdot R \cdot C} \right) - \frac{\pi}{2}$$

$$A = \frac{2 \cdot \pi \cdot R \cdot C}{\sqrt{(2 \cdot \pi \cdot f \cdot R \cdot C)^2 + 1}}$$

$$\phi = \text{atan} \cdot \left(\frac{1}{2 \cdot \pi \cdot f \cdot R \cdot C} \right) - \frac{\pi}{2}$$