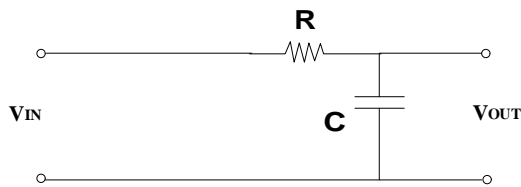



# RC Filter Circuits, Waveforms

By: S.E. Van Bramer. 1/15/98

Low Pass Filter



High Pass Filter

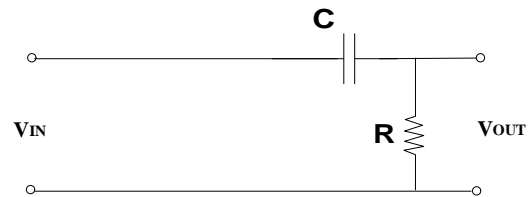

Constants and Definitions:

$$k \equiv 1000 \cdot \text{ohm} \quad \text{kHz} := 1000 \cdot \text{Hz} \quad \text{MHz} := 10^6 \cdot \text{Hz} \quad \mu\text{F} := 10^{-6} \cdot \text{farad} \quad \text{dB}(x) := 20 \cdot \log(x)$$

Variables

$$V_{\text{in}} := 1 \cdot \text{volt} \quad R \equiv 5 \cdot k \quad C \equiv 1 \cdot \mu\text{F} \quad \text{frequency} \equiv 100 \cdot \text{Hz}$$

Calculated Paramters

$$R \cdot C = 0.005 \cdot \text{sec} \quad \frac{1}{2 \cdot \pi \cdot R \cdot C} = 31.831 \cdot \text{Hz}$$

Equations for RC Filters:

$$A_{\text{HP}}(f) := \frac{(2 \cdot \pi \cdot f) \cdot R \cdot C}{\sqrt{(2 \cdot \pi \cdot f)^2 \cdot R^2 \cdot C^2 + 1}} \quad \text{Amplitude of high pass filter}$$

$$A_{\text{LP}}(f) := \frac{1}{\sqrt{(2 \cdot \pi \cdot f)^2 \cdot R^2 \cdot C^2 + 1}} \quad \text{Amplitude of low pass filter}$$

$$\phi_{\text{HP}}(f) := \text{atan} \left[ \frac{1}{(2 \cdot \pi \cdot f) \cdot R \cdot C} \right] \quad \text{Phase of high pass filter}$$


$$\phi_{\text{LP}}(f) := \left[ -\text{atan} \left[ \frac{-1}{(2 \cdot \pi \cdot f) \cdot R \cdot C} \right] - \frac{\pi}{2} \right] \quad \text{Phase of low pass filter}$$

$$t_{\text{scope}} := 0 \cdot \text{sec}, \frac{5}{\text{frequency} \cdot 500} \dots \frac{5}{\text{frequency}}$$

$$V_{\text{signal}}(t) := \sin((2 \cdot \pi \cdot \text{frequency}) \cdot t)$$

$$V_{\text{LP}}(t) := A_{\text{LP}}(\text{frequency}) \cdot \sin \left[ (2 \cdot \pi \cdot \text{frequency}) \cdot t + \phi_{\text{LP}}(\text{frequency}) \right]$$
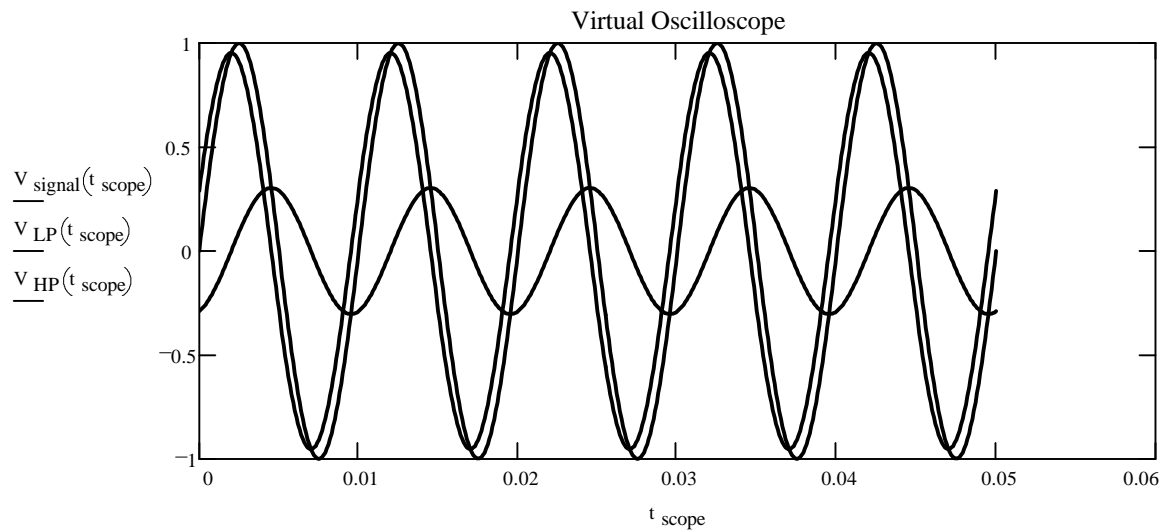
$$V_{\text{HP}}(t) := A_{\text{HP}}(\text{frequency}) \cdot \sin \left[ (2 \cdot \pi \cdot \text{frequency}) \cdot t + \phi_{\text{HP}}(\text{frequency}) \right]$$



Circuit Gain:

Low Pass  $A_{\text{LP}}(\text{frequency}) = 0.303$

High Pass  $A_{\text{HP}}(\text{frequency}) = 0.953$

Circuit Gain (in decibals):

Low Pass  $\text{dB}(A_{\text{LP}}(\text{frequency})) = -10.362$

High Pass  $\text{dB}(A_{\text{HP}}(\text{frequency})) = -0.419$

Circuit Phase Shift:

Low Pass  $\phi_{\text{LP}}(\text{frequency}) = -0.402 \cdot \pi \cdot \text{rad}$   $\phi_{\text{LP}}(\text{frequency}) = -72.343 \cdot \text{deg}$

High Pass  $\phi_{\text{HP}}(\text{frequency}) = 0.098 \cdot \pi \cdot \text{rad}$   $\phi_{\text{HP}}(\text{frequency}) = 17.657 \cdot \text{deg}$